

DIGITAL LOGIC DESIGN

ECE2002

Tutorial -1

Dr. Anirban Bhowmick

1. Simplify the following Boolean expressions to a minimum number of literals:

(a) $xy + xy'$	(b) $(x + y)(x + y')$
(c) $xyz + x'y + xyz'$	(d) $(A + B)'(A' + B')'$
(e) $(a + b + c')(a'b' + c)$	
(f) $a'bc + abc' + abc + a'bc'$	

2. Reduce the following Boolean expressions to the indicated number of literals:

(a) $A'C' + ABC + AC'$	to three literals
(b) $(x'y' + z)' + z + xy + wz$	to three literals
(c) $A'B(D' + C'D) + B(A + A'CD)$	to one literal
(d) $(A' + C)(A' + C')(A + B + C'D)$	to four literals
(e) $ABC'D + A'BD + ABCD$	to two literals

3. Draw logic diagrams of the circuits that implement the original and simplified expressions in Problem 2 (a).

4. Find the complement of $F = wx + yz$; then show that $FF' = 0$ and $F + F' = 1$.

5. Find the complement of the following expressions:

- $xy' + x'y$
- $(a + c)(a + b')(a' + b + c')$
- $z + z'(v'w + xy)$

6. Implement the Boolean function:

$$F = xy + x'y' + y'z \text{ with AND, OR, and inverter gates}$$

7. The logical sum of all *minterms* of a Boolean function of n variables is 1. Prove the previous statement for $n = 3$.

8. Express the following function as a sum of *minterms* and as a product of *maxterms*:

$$F(A, B, C, D) = B'D + A'D + BD$$

9. Express the complement of the following functions in sum-of-minterms form:

a. $F(A, B, C, D) = \sum(2, 4, 7, 10, 12, 14)$

b. $F(x, y, z) = \prod(3, 5, 7)$

10. Convert each of the following to the other canonical form:

a. $F(x, y, z) = \sum(1, 3, 5)$

b. $F(A, B, C, D) = \prod(3, 5, 8, 11)$


11. Convert each of the following expressions into sum of products and product of sums:

a. $(u + xw)(x + u'v)$

b. $x + x(x + y)(y + z')$

12. Show that the dual of the exclusive-OR is equal to its complement.

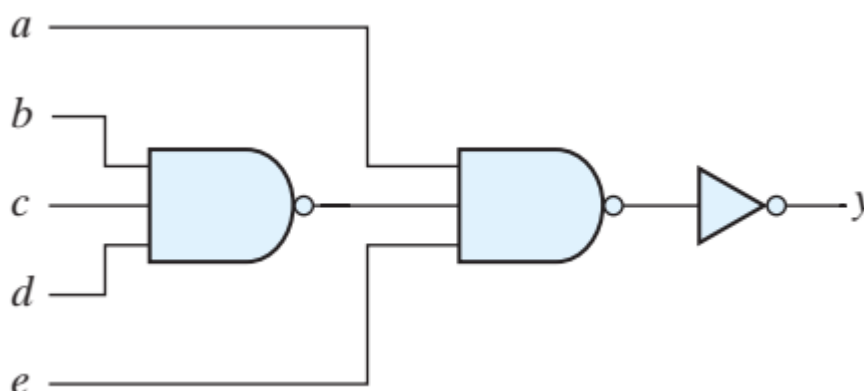13. Write Boolean expressions and construct the truth tables describing the outputs of the circuits described by the logic diagrams as shown below:



14. Write Boolean expressions and construct the truth tables describing the outputs of the circuits described by the logic diagrams as shown below:

