

Reg. No.:

Name :




VIT[®]
BHOPAL
www.vitbhopal.ac.in

Mid-Term Examinations – October 2021

Programme	: B.Tech	Semester	: Fall 2021-22
Course	: Electric Circuits and Systems	Code	: EEE1001
Faculty	: Dr. Abhishek Joshi	Slot/ Class No.	: D11+D12+D13/0602
Time	: 1 ½ hours	Max. Marks	: 50

Answer all the Questions


Q.No.	Sub. Sec.	Question Description	Marks
1	(a)	Find the value of current I in the circuit.	5
	(b)	Find the current through each diode in the circuit shown in Figure. Assume diodes are made of Silicon with no internal resistance.	5
2	(a)	Find the voltage across resistance R ₁ using mesh analysis.	5
	(b)	Use De Morgan's law to simplify the following expression: ((A' + C) (B + D'))'	5
3	(a)	For the BJT circuit shown in the Figure, Find the values of I _C and I _E .	5

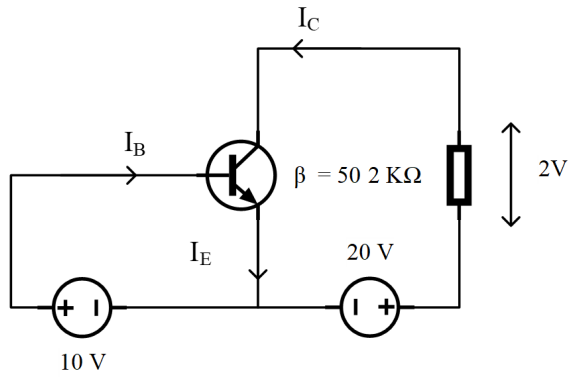

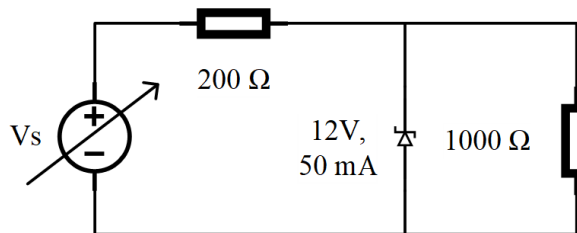- (b) Convert decimal fraction (0.865) into its Binary, Decimal and Octal equivalent. Mention conversion steps.


5

- 4 Find the minimum and maximum values of source voltage can be applied to obtain regulated voltage output through Zener diode.



10

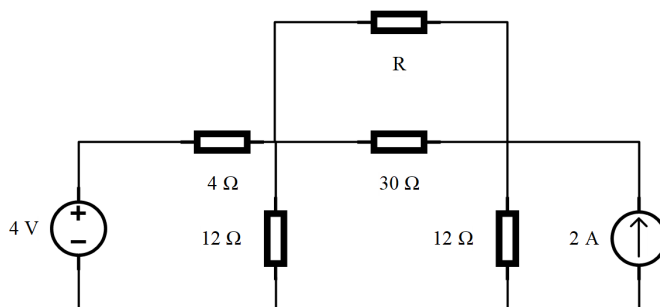- 5 For the circuit shown in Figure, find the Thevenin equivalent as viewed by the resistance R. Find the value of R for maximum power dissipation in it and the value of the power.



10

