

# LAB ASSESSMENT (CHALLENGING TASK)

## ELECTRICAL CIRCUITS AND SYSTEMS

EEE1001

D11+D12+D13

*BACHELOR OF TECHNOLOGY*

*SCHOOL OF COMPUTING SCIENCE AND  
ENGINEERING*



**VIT<sup>®</sup>**  
**BHOPAL**  
[www.vitbhopal.ac.in](http://www.vitbhopal.ac.in)

*Class Number:* **BL2021221000162**

*Faculty name:* **MOHAMMAD SARWAR RAEEN**


*Submitted by:* ***Fiza Siddiqui***

*Registration Number:* **20BCE10077**


*Dated:* **23/12/2021**

*Session:* **2021-2022 (fall semester)**


# 1.BCD TO GRAY CODE

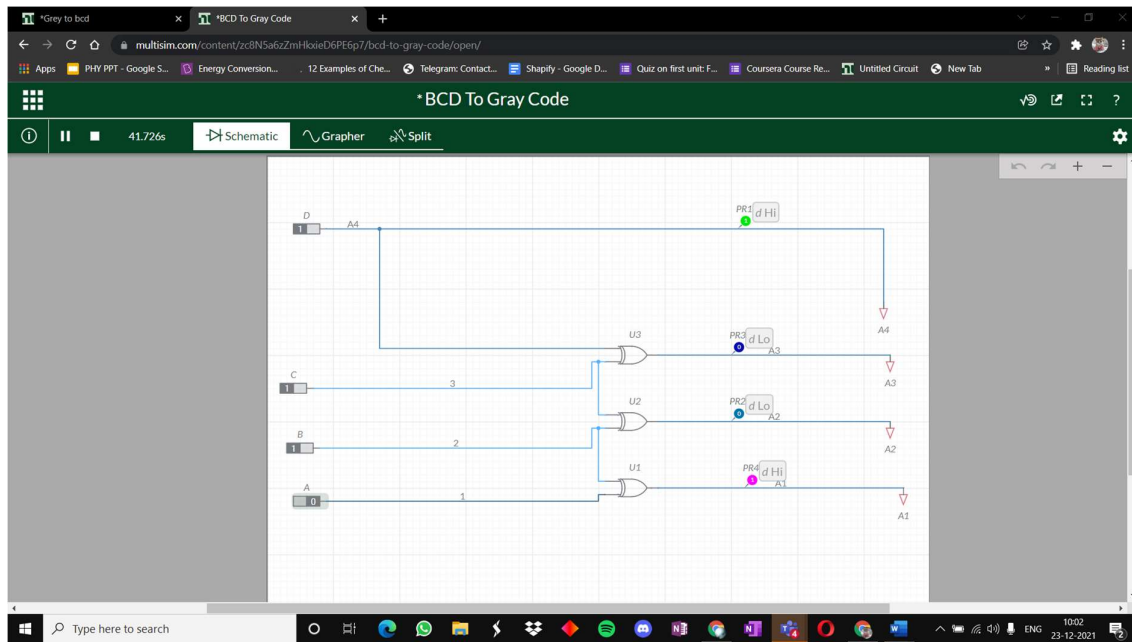


1

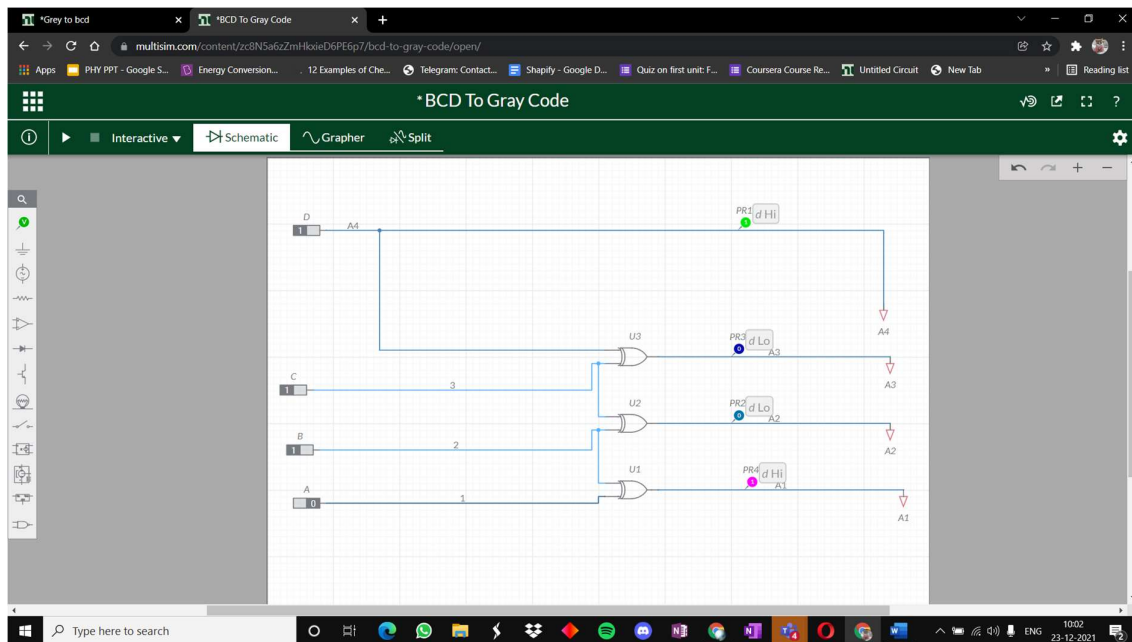


2

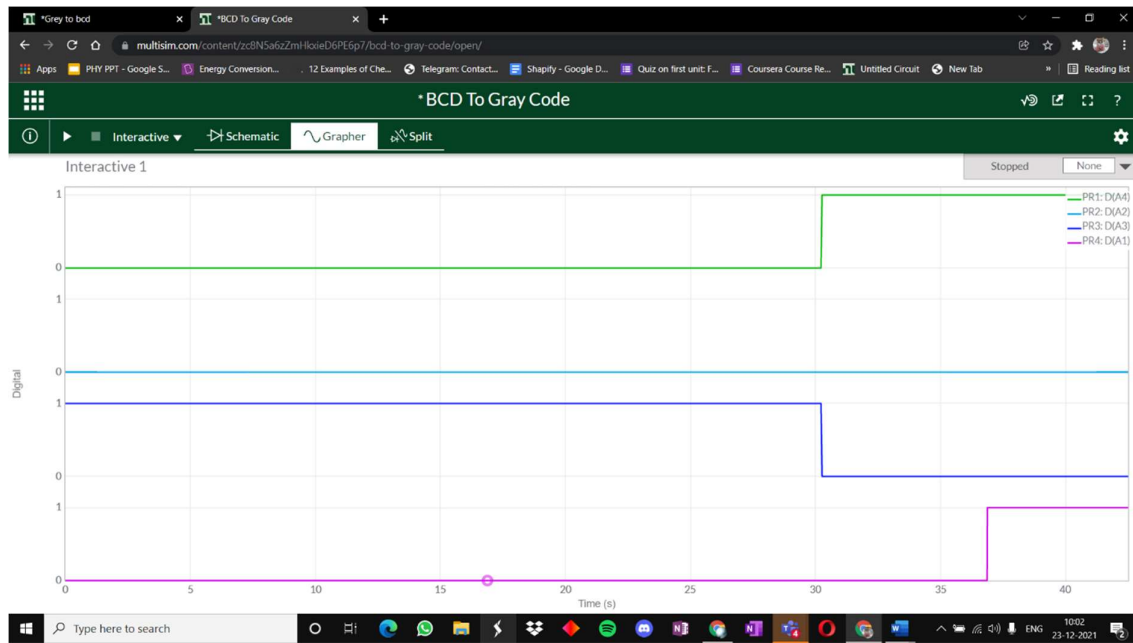


## 2. GREY CODE TO BCD

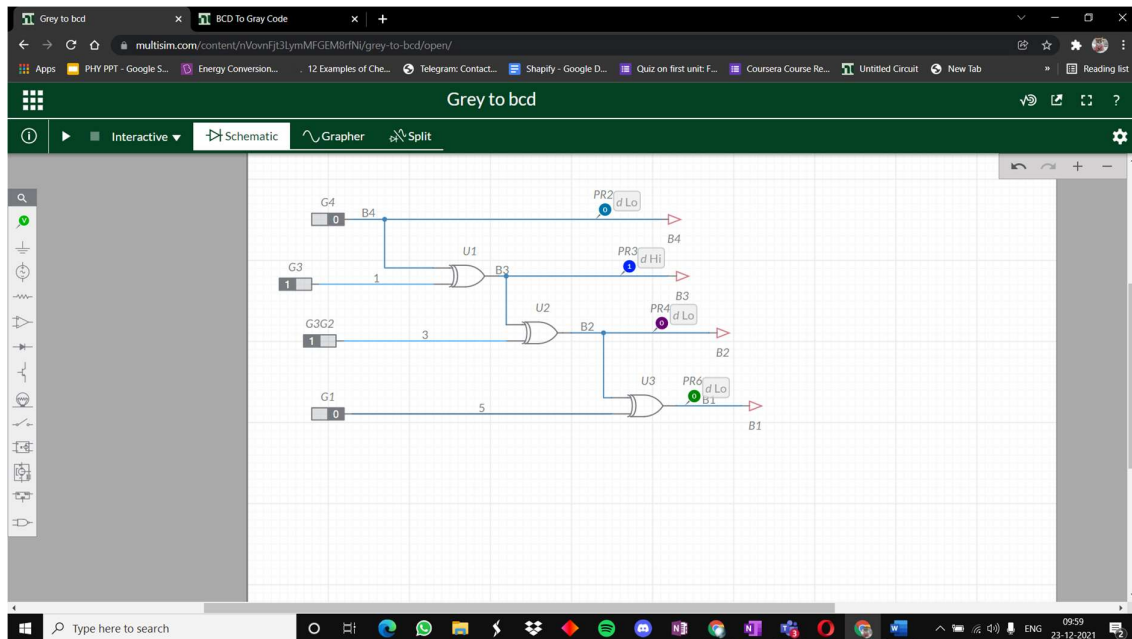


1

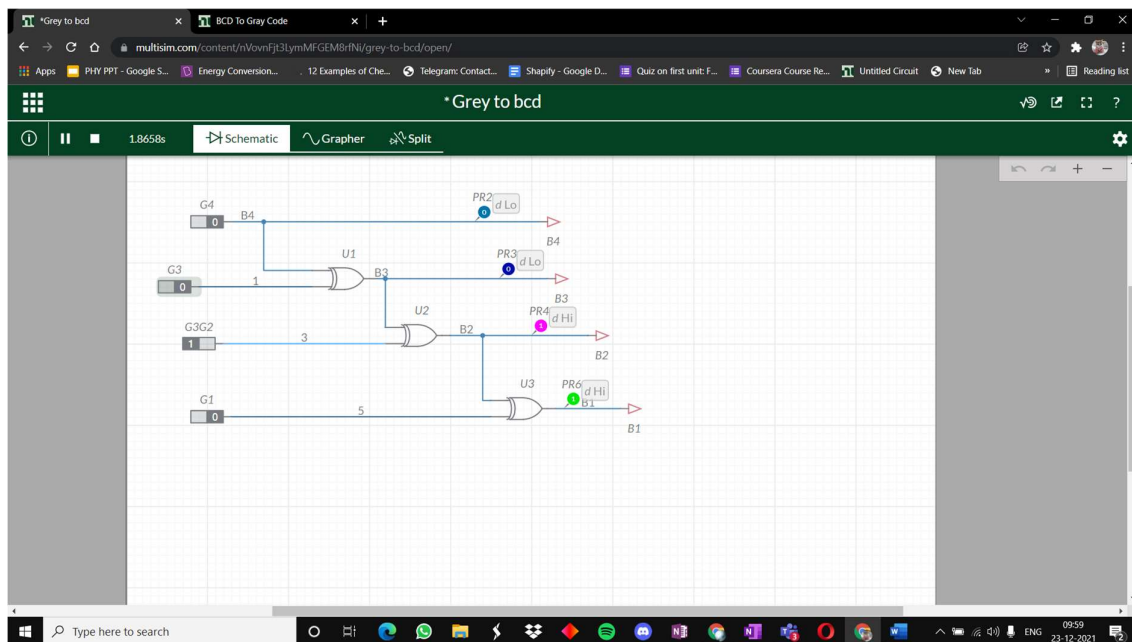

2

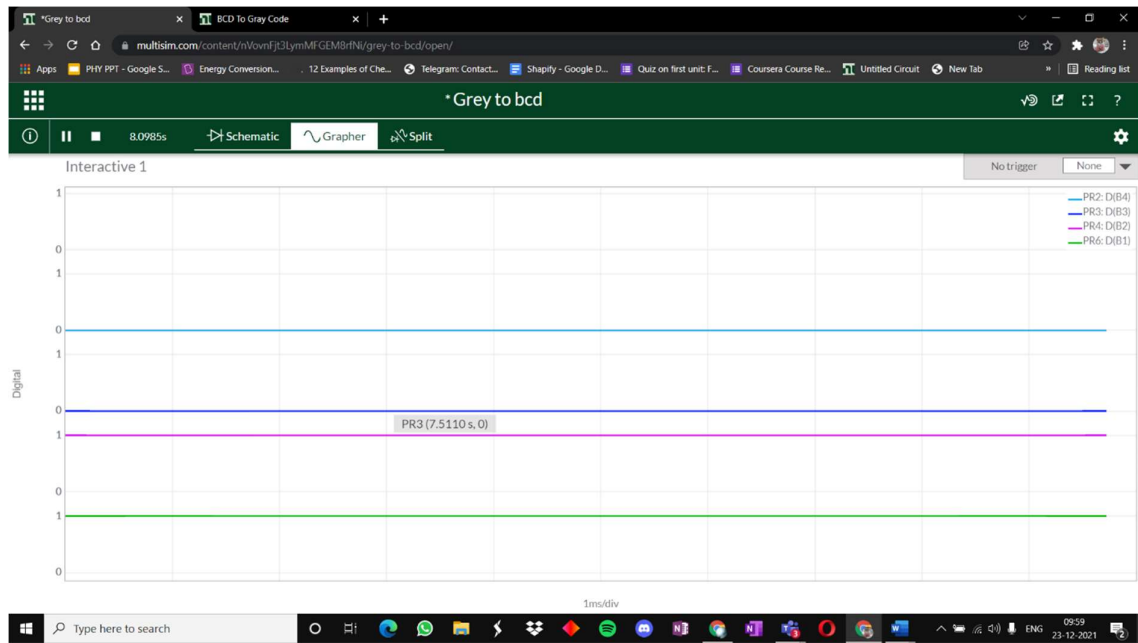

3

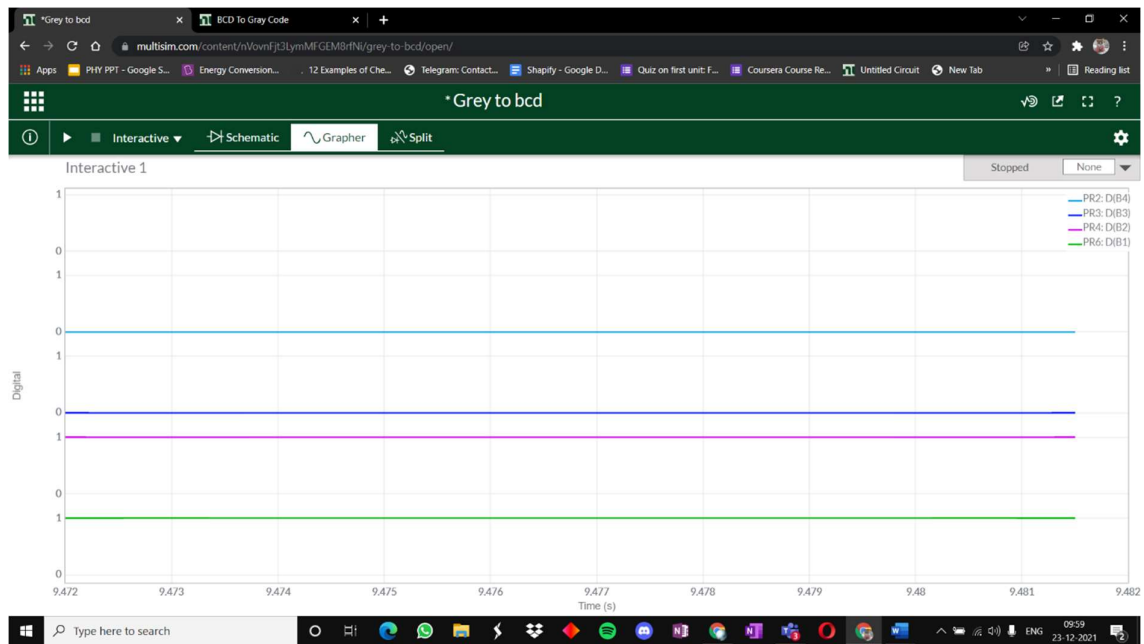

4