

Reg. No.:

Name :



VIT[®]
BHOPAL
www.vitbhopal.ac.in

Mid-Term Examinations, April 2021

Programme	: B.Tech	Semester	: Winter 2020-2021
Course	: Digital Logic Design	Code	: ECE2002
Faculty	: Dr. Anirban Bhowmick	Slot/Class No.	: D11+D12+D13/0377
Time	: 1½ hours	Max. Marks	: 50

Answer all the Questions

Q. No.	Question Description	Marks
1	(i) Design a 3 bit combinational circuit which produce logic '1' when more than one input variables are at logic '1'. (ii) Show that $AB'C + B + BD' + ABD' + A'C = B + C$.	5 5
2	(i) A Boolean function, F is given by the minterms as $f(A,B,C)=\sum m(3,4,5,6)$. Implement this function on 4:1 MUX by considering AC as your selection lines. (ii) Design a multiplier which can perform the multiplication of two numbers $(5)_{10} \times (3)_{10}$.	4 6
3	(i) Minimize the following function using K-MAP: $F = \sum m(0,2,6,10,11,12,13) + d(3,4,5,14,15).$ (ii) Convert decimal 27.315 to binary.	7 3
4	(i) In a J K flip flop, we have $J = Q'$ and $K = 1$. Assume the flip flop was initially cleared and then clocked for 6 pulses, find the sequence at the Q after 6 pulse (Fig. 1).	6

 


Fig.1

(ii) Design a Half adder using 2×4 Decoder

4

5 (i) Design a J K flip flop from a S R flip flop.

5

(ii) A sequential circuit using D flip-flop and logic gates is shown in the Fig.2, calculate the output for 4 clock cycle when you apply. $X=1$ and $Y=1$ and the clock is a negative edge trigger. Assume that initially the flip flop is cleared.

5

 


Fig.2

