

DIGITAL LOGIC DESIGN

ECE2002

Tutorial -2

Dr. Anirban Bhowmick

1. K-Map reduction

a) $F(A,B,C,D) = \sum m(2,3,6,7,10,11,14)$

b) $F(w,x,y,z) = \prod M(1,3,4,6,8,9,14,15)$

c) $F(A,B,C,D) = \sum m(1,4,7,10,12,14) + \sum d(2, 6,11,13)$

d) $F(A,B,C,D,E) = \sum m(1,2,3,8,10,17,19,23,25,27,29,31) + \sum d(4, 7,20,24)$

2. A safe has 5 locks v, w, x, y and z all of which must be unlocked the safe to open. The keys to the locks are distributed among five executives in the following manner.

Mr. A has keys for locks v and x.

Mr. B has keys for locks v and y.

Mr. C has keys for locks w and y.

Mr. D has keys for locks x and z.

Mr. E has keys for locks v and z.

a) Determine the minimal number of executives required to open the safe.

b) Find all the combinations of executives that can open the safe, write an expression $f(A, B, C, D, E)$ which specifies when the safe can be opened as a function of what executives are present.

c) Who is the essential executive?

3. You are presented with a set of requirements under which an insurance policy can be issued. The applicant must be:

i) A married female 25 years old or over, or

ii) A female under 25, or

iii) A married male under 25 who has not been involved in a car accident, or

iv) A married male who has been involved in a car accident, or

- v) A married male 25 years or over who has not been involved in a car accident.

Find an algebraic expression which assumes a value 1 whenever the policy is issued. Simplify the expression obtained.

4. Design a Full adder circuit with two 4:1 Multiplexer.
5. Design a 3 bit Gray to Binary Converter.
6. Design an odd parity generator and checker.